

I had no Partner on
this project

Question 1

1).

$$V_1 = 150 \angle -5^\circ V$$

$$V_2 = 120 \angle 0^\circ V$$

$$R + jx = 1 + j8 \Omega$$

$$-5^\circ < 0^\circ$$

Project 1

$$Z = 4 + j8 \Omega$$

Graham Robinson

$$I_{z_1} = \frac{V_2 - V_1}{Z} = \frac{(120 + j0) - (149.43 - j13.07)}{(4 + j8)} =$$

$$I_{z_1} = -0.16 + j3.8 = 3.8 \angle -87.48^\circ A$$

$$a). S = V - I_{z_1}^* \rightarrow S_1 = V_1 - I_{z_1}^* = (150 \angle -5^\circ)(-3.6 \angle 87.96^\circ)$$

$$S_1 = -540 \angle 82.96^\circ VA = -70.86 - j535.33 VA$$

$$P_1 = -70.86 V$$

$$Q_1 = -535.33 VAR$$

$$S_2 = V_2 I^* = (120 \angle 0^\circ)(3.6 \angle 87.96^\circ)$$

$$S_2 = 432 \angle 87.96^\circ VA = 17.14 + j431.58 VA$$

$$P_2 = 17.14 W$$

$$Q_2 = 431.58 VAR$$


$$b). P_{loss} = R |I_{z_1}|^2 = 4 |3.6|^2 = 51.84 W$$


$$Q_{loss} = X |I_{z_1}|^2 = 8 |3.6|^2 = 103.68 VAR$$


c). Matlab 3 Graphs Images Below

d). Matlab 1 Graph

As well as
Zip File

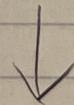

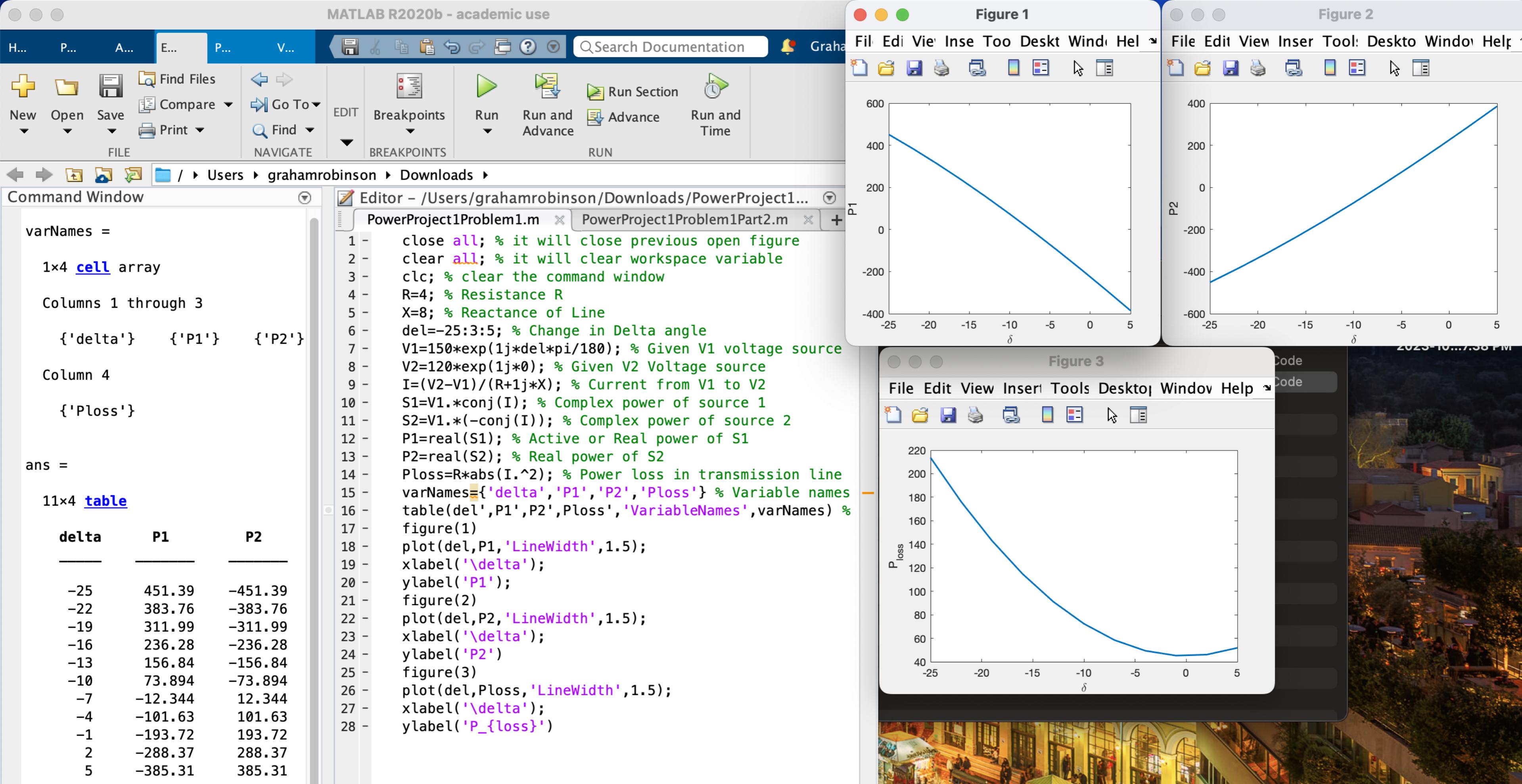

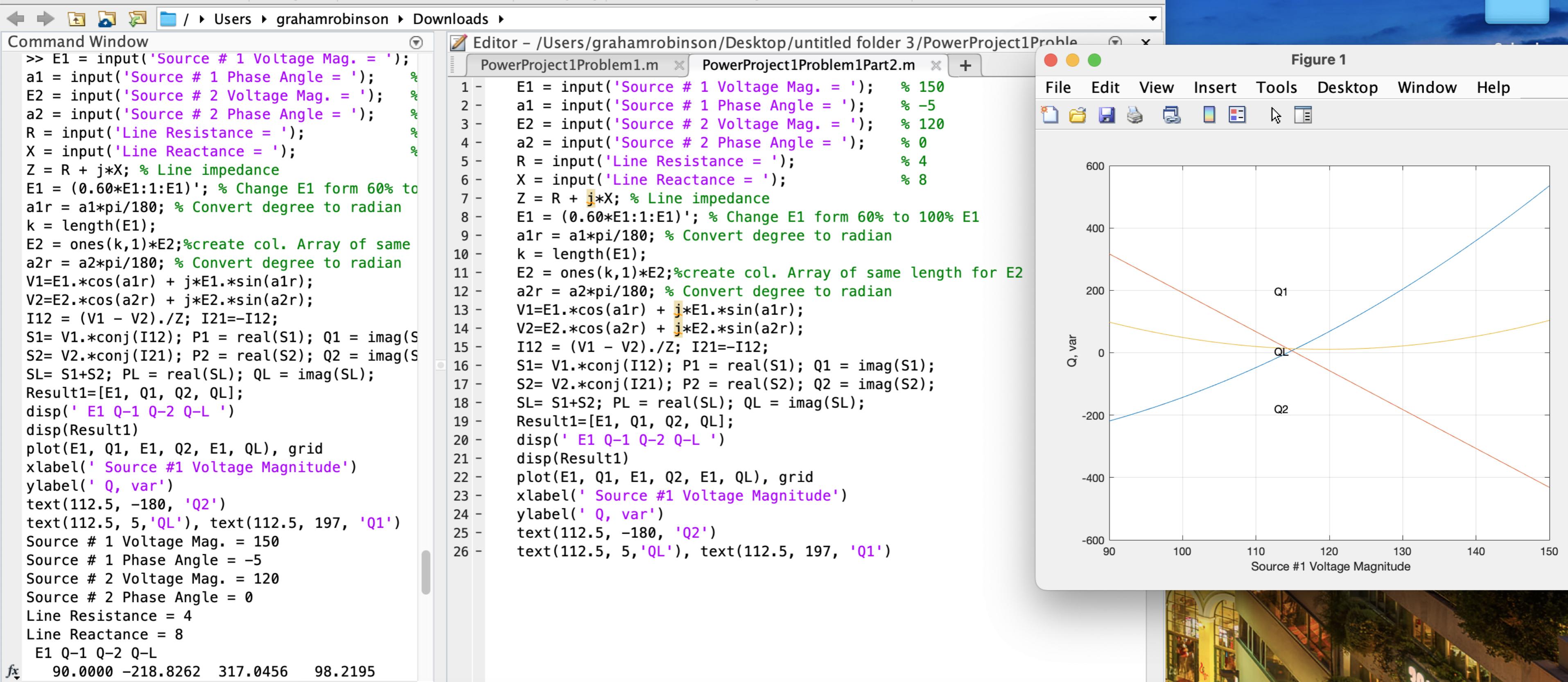



Question 2

$$2), \quad V_{an} = 141 + \cos(120\pi t) V \quad ZY = 300 - j400$$

$$V_{bn} = 141 + \cos(120\pi t - 120^\circ) V \quad Z\Delta = 3000 \angle 53^\circ$$

$$V_{cn} = 141 + \cos(120\pi t - 240^\circ) V \quad Z\Delta = \frac{ZY}{s} = 1000 \angle 53^\circ \text{ N}$$

a).

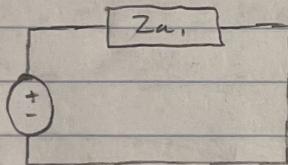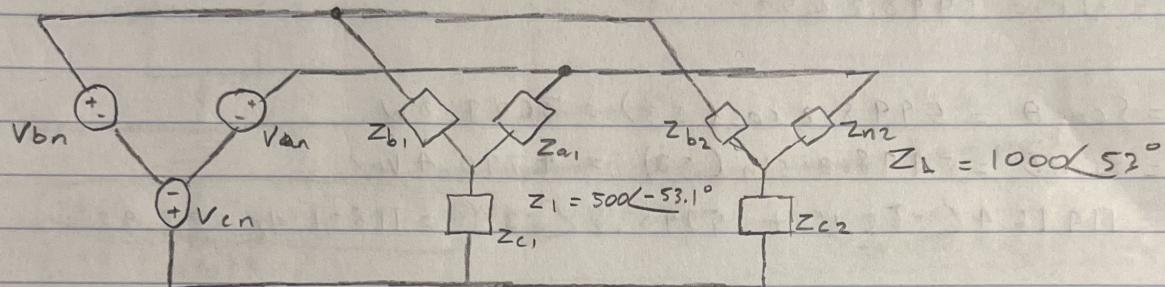

$$Z = \frac{V}{I} \quad I = \frac{V}{Z} \quad 141 + \angle 0^\circ$$


$$I_{a1} = 2.83 \angle -53.1^\circ \quad I_{a1} = 500 \angle -53.1^\circ$$

$$S_P = V \angle 0^\circ = (141 + \angle 0^\circ)(2.83 \angle -53.1^\circ) = 3998.8 \angle -53.1^\circ$$

$$S_T = 3S_P = 11996.4 \angle -53.1^\circ$$

$$P = S \cos \theta = 11996.4 \cos(-53.1) = 7202.9 \text{ W}$$
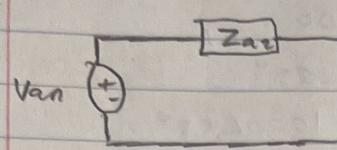
$$Q = S \sin \theta = 11996.4 \sin(-53.1^\circ) = -9593.3 \text{ var}$$



$$I_{a2} = \frac{1414 \angle 0^\circ}{1000 \angle 53^\circ} = 1.414 \angle -53^\circ A$$

$$S = VI^* = (1414 \angle 0^\circ)(1.414 \angle -53^\circ) = 1999.4 \angle -53^\circ VA$$

$$ST = 3SP = 5998.2 \angle 53^\circ$$

$$P = S \cos \theta = 5998.2 \cos(53) = 3609.8 W$$

$$Q = S \sin \theta = 5998.2 \sin(53) = 4790.4 \text{ var}$$

$$ST = 11996.4 \angle -53.1^\circ + 5998.2 \angle 53^\circ = 11831.4 \angle -23.95^\circ$$


$$PT = 7202.4 + 3609.8 = 10812.7 W$$

$$QT = -9593.3 + 4790.4 = -4803.0 W$$

b). $I_T = 3(I_{a1} + I_{a2}) = 3(2.83 \angle 53.1^\circ + 1.414 \angle -53^\circ) = 8.37 \angle 23.97^\circ A$

$$IL_1 = 3I_{a1} = 3(2.83 \angle 53.1^\circ) = 7.00 \angle 75.95^\circ A$$

$$IL_2 = 3I_{a2} = 3(1.414 \angle -53^\circ) = 4.24 \angle -53^\circ A$$

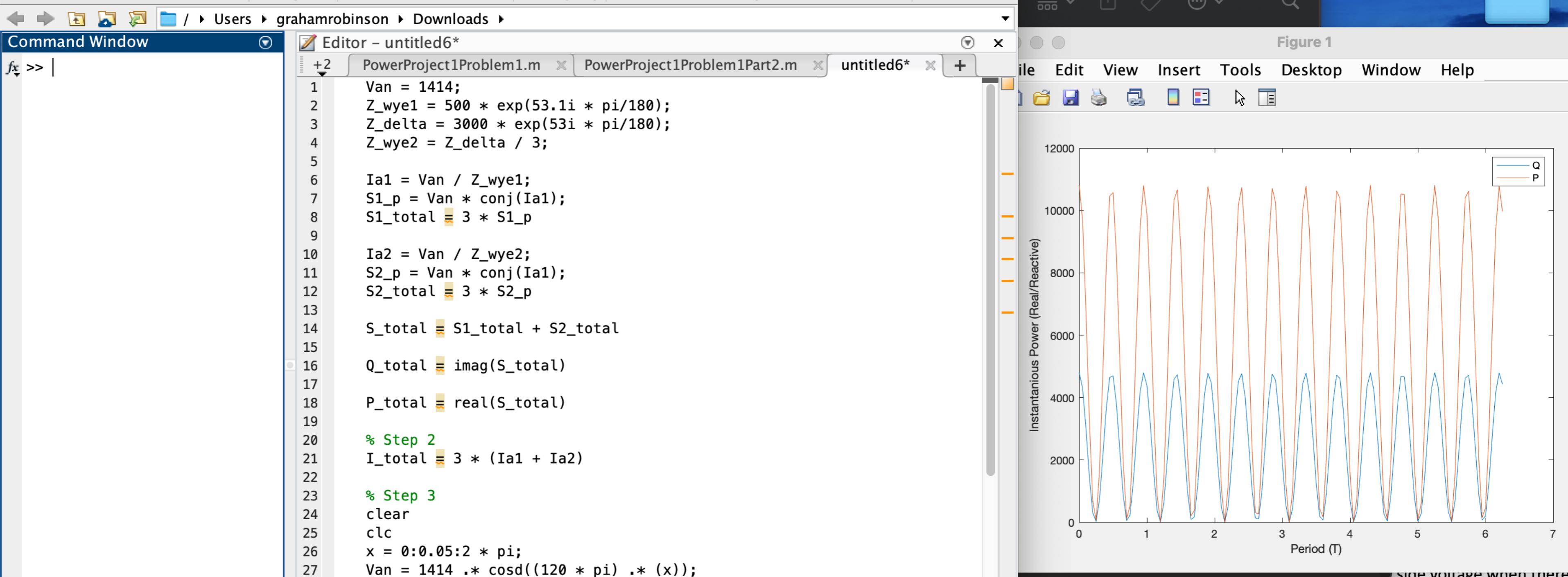


Question 3

3). $a = \frac{2400}{240} = 10 \quad S = 150 \text{ kVA}$

a). $Z_{eq} = (0.2 + j0.45) + (10)^2 (0.002 + j0.0045) = 0.4 + j0.9 \Omega$

$S = (150 \times 10^3) \angle \cos^{-1}(0.8) = (150 \times 10^3) \angle -36.87^\circ \text{ VA}$

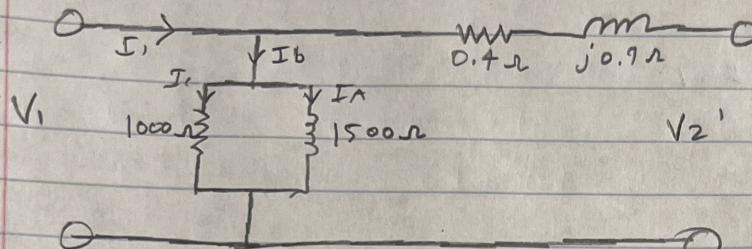$P = 119,999.84 \text{ W} \quad Q = 90,000.21 \text{ VAR}$



$$R_{eq} = 0.2 + 0.2 \\ = 0.4 \Omega$$

$$X_{eq} = 0.45 + 0.45 \Omega \\ = j0.9$$


b). $Z_{eq} = \frac{(0.2 + j0.45)}{(10)^2} + (0.002 + j0.0045)$

$$= 0.004 + j0.009 \Omega$$

$$R_C' = \frac{1000}{10^2} = 10 \Omega$$

$$X_M' = \frac{1500}{10^2} = 15 \Omega$$

$$Z_{eq} = (0.4 + j0.9) \Omega$$

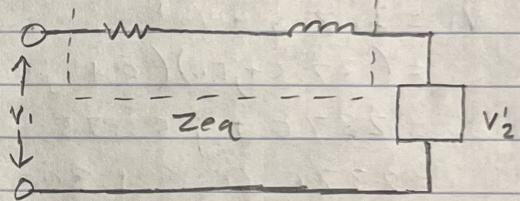

c). $\cos \phi = 0.8 \quad \phi = \cos^{-1}(0.8) = 36.87^\circ$

$$V_2' = 10 \times 240 = 2400 \text{ V}$$

$$S = P \cos \phi + j Q \sin \phi$$

$$= 150 \cos 36.87 + j 150 \sin 36.87$$

$$= (120 + j90) \text{ kVA}$$

$$I_1 = \frac{S}{V_2'} = \frac{(120 - j90)}{2400} = (50 - j37.5) \text{ A}$$

$$V_1 = I_1 \times Z_{eq} + V_2'$$

$$= (50 - j37.5)(0.4 + j0.9) + 2400$$

$$= 53.75 + j30 + 2400$$

$$= 2453.75 + j30$$

$$= 2454 \angle 0.7^\circ \text{ V}$$

$$V_{reg} = \frac{|V_1| - |V_2'|}{|V_2'|} = \frac{2454 - 2400}{2400} \times 100 = 2.25\%$$

d) $\cos \phi = 0.6$

$$\phi = \cos^{-1}(0.6)$$

$$= 53.13^\circ$$

$$S = P \cos \phi - j Q \sin \phi$$

$$= 150 \cos 53.13 - j 150 \sin 53.13$$

$$= (90 - j 120) \text{ kVA}$$

$$I_1 = \frac{S^*}{V_2'} = \frac{(40 + j120)}{2400}$$

$$= (37.5 + j50) \text{ A}$$

$$V_1 = I_1 Z_{eq} + V_2'$$

$$= (37.5 + j50)(0.4 + j0.9) + 2400$$

$$= 2370 + j53.75$$

$$= 2370.60 \angle 1.30^\circ \text{ V}$$

$$V_{reg} = \frac{|V_1| - |V_2'|}{|V_2'|}$$

$$= \frac{2371 - 2400}{2400} \times 100$$

$$= -1.21\%$$

e). Matlab

